


VHDL CODE DEVELOPMENT AND CPLD BOARD OPERATING

Aim: The purpose is to create VHDL code, feed it to a CPLD board, and test the board's operation.

Summary Of the Experiment: Creating structural VHDL code for a 3-bit universal shift register using behavioral VHDL code for a D flip flop and MUX, then putting it into a CPLD board to test its functionality.


Components Used: CPLD MAX3000A Board, JTAG port, Type-B USB cable, ALTERA BUS Blaster cable, and Bus Blaster HDL code were the components utilized (for CPLD).

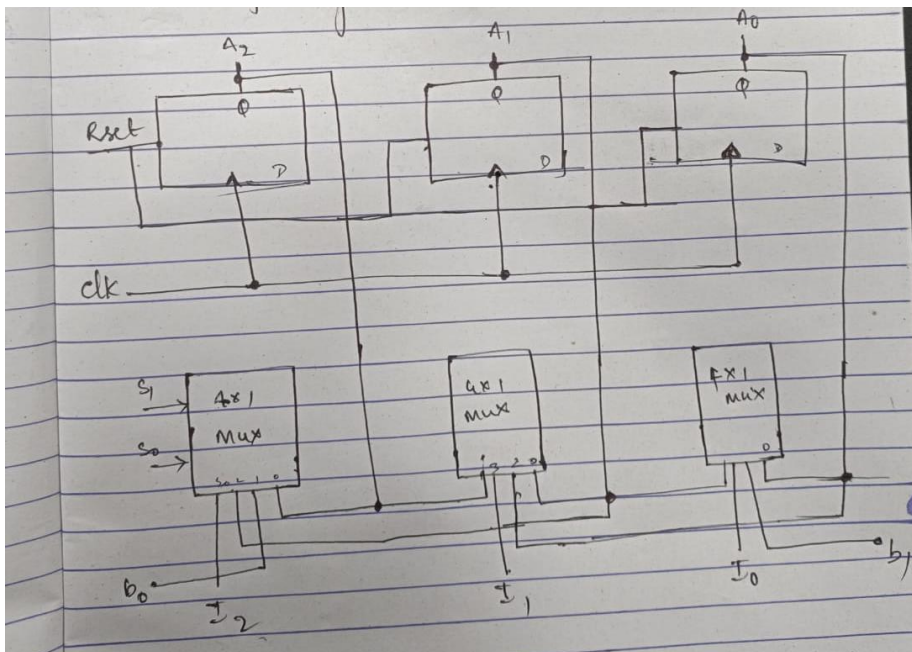Circuit Diagram: 3-bit Universal Shift Register



Snapshots Of Gate-level Netlist:

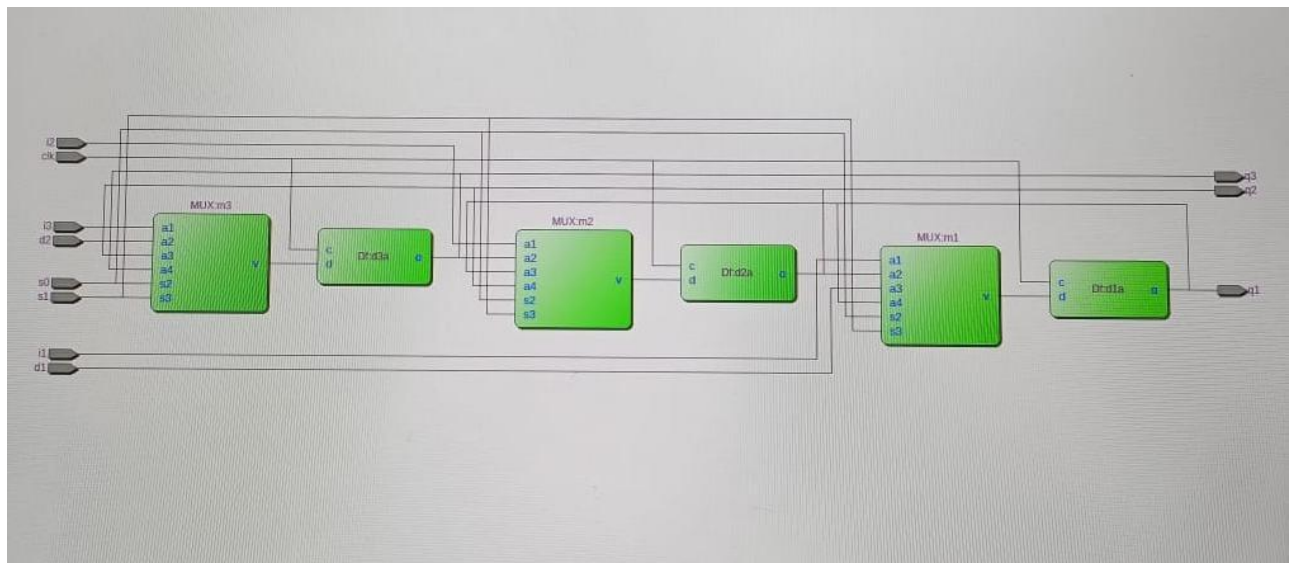3-bit Universal Shift Register in structural modeling style



VHDL Code:

3-bit Universal Shift Register in structural modeling style


```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity shift_register is
5  port (s1,s0,i1,i2,i3,d1,d2,clk:in std_logic;
6        q1,q2,q3:out std_logic);
7  end shift_register;
8
9  architecture structure of shift_register is
10 component Df
11 port (d,c: in std_logic;
12       q: out std_logic);
13 end component;
14 component MUX
15 port (s2,s3,a1,a2,a3,a4: in std_logic;
16       y:out std_logic);
17 end component;
18 signal c1,c2,c3,c4,y1,y2,y3 : std_logic;
19 begin
20 m1:MUX port map(s0,s1,i1,c1,d1,c2,y1);
21 m2:MUX port map(s0,s1,i2,c4,c2,c1,y2);
22 m3:MUX port map(s0,s1,i3,d2,c1,c4,y3);
23 d1a: Df port map(y1,clk,c2);
24 d2a: Df port map(y2,clk,c1);
25 d3a: Df port map(y3,clk,c4);
26 q1<=c2;
27 q2<=c1;
28 q3<=c4;
29 end structure;
30
31 library IEEE;
32 use IEEE.STD_LOGIC_1164.ALL;
33
34 entity Df is
35 port (d,c,rst:in std_logic;
36       q:out std_logic);
37 end Df;
38
39 architecture Behavioral of Df is
40 begin
41 process(rst,c)
42 begin
43
44 if (rst='1') then
```

```

46     q<='0';
47   elsif(c'event and c='1') then
48   q<=d;
49   end if;
50 end process;
51 end Behavioral;
52
53
54 library IEEE;
55 use IEEE.STD_LOGIC_1164.ALL;
56 entity MUX is
57 port (s2,s3,a1,a2,a3,a4: in std_logic;
58       y:out std_logic);
59 end MUX;
60 architecture behavioral of MUX is
61 begin
62 process (s2,s3)
63 begin
64   if(s2='0' and s3='0') then
65     y<=a1;
66   elsif(s2='1' and s3='0') then
67     y<=a2;
68   elsif(s2='0' and s3='1') then
69     y<=a3;
70   elsif(s2='1' and s3='1') then
71     y<=a4;
72   end if;
73 end process;
74 end behavioral;

```

CPLD Board Image:

 

Results and Conclusion: Acquired a thorough understanding of how to create VHDL code using the circuit's logic. By loading the code onto a CPLD board, the 3-bit Universal Shift Register's functioning was tested using this information to construct the code.