

LAB 2 REPORT:

STIMULATION OF CMOS AS LOGIC GATES

Aim: Study of HCC4007UB & HCF400UB ICs and basic components like power supply, DSO etc.

Summary of the experiment: Study of HCC4007UB and HCF400UB verifying their functionality, learning the usage of function generator (FG) and digital storage and how that works as CMOS by two NMOS & PMOS

Components used: HCC4007UB and HCF400UB IC's 1Kohm resistor array -2 , DIP switches, LED displays, breadboard, power supply.

Design Procedure & circuit gates :


Truth table/Excitation table of all logic gates and logic circuits.

Truth tables are written below for :


- 1) NAND Gate
- 2) AND Gate
- 3) NOR Gate
- 4) OR Gate

REPRESENTATION OF TRANSISTORS :


PMOS & NMOS :

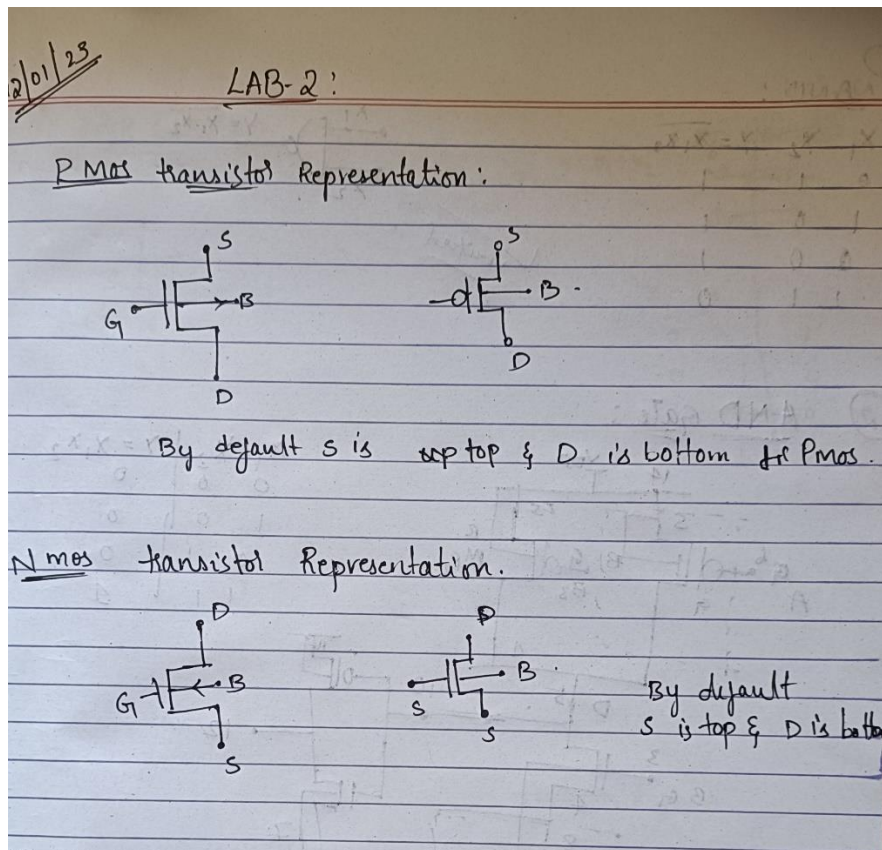

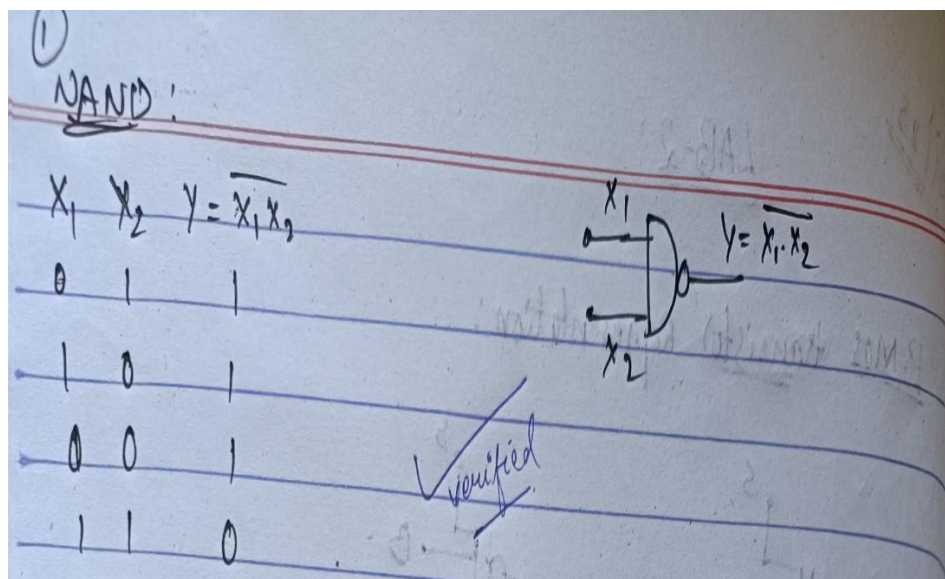
1) NAND GATE (Snapshots) : TRUTH TABLE & CIRCUIT :





(1) NAND - GATE

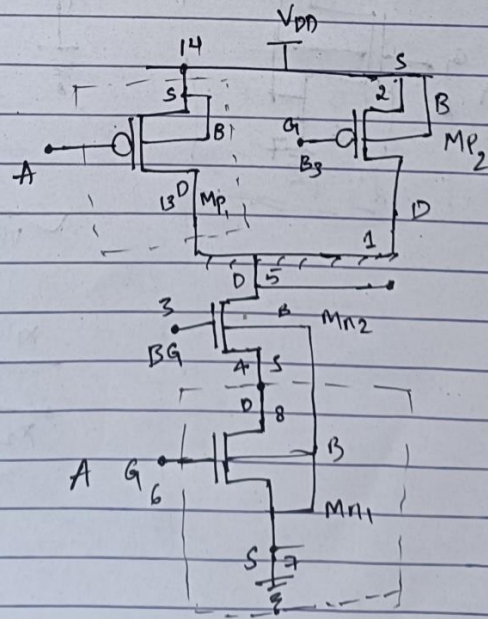



2 - NAND.

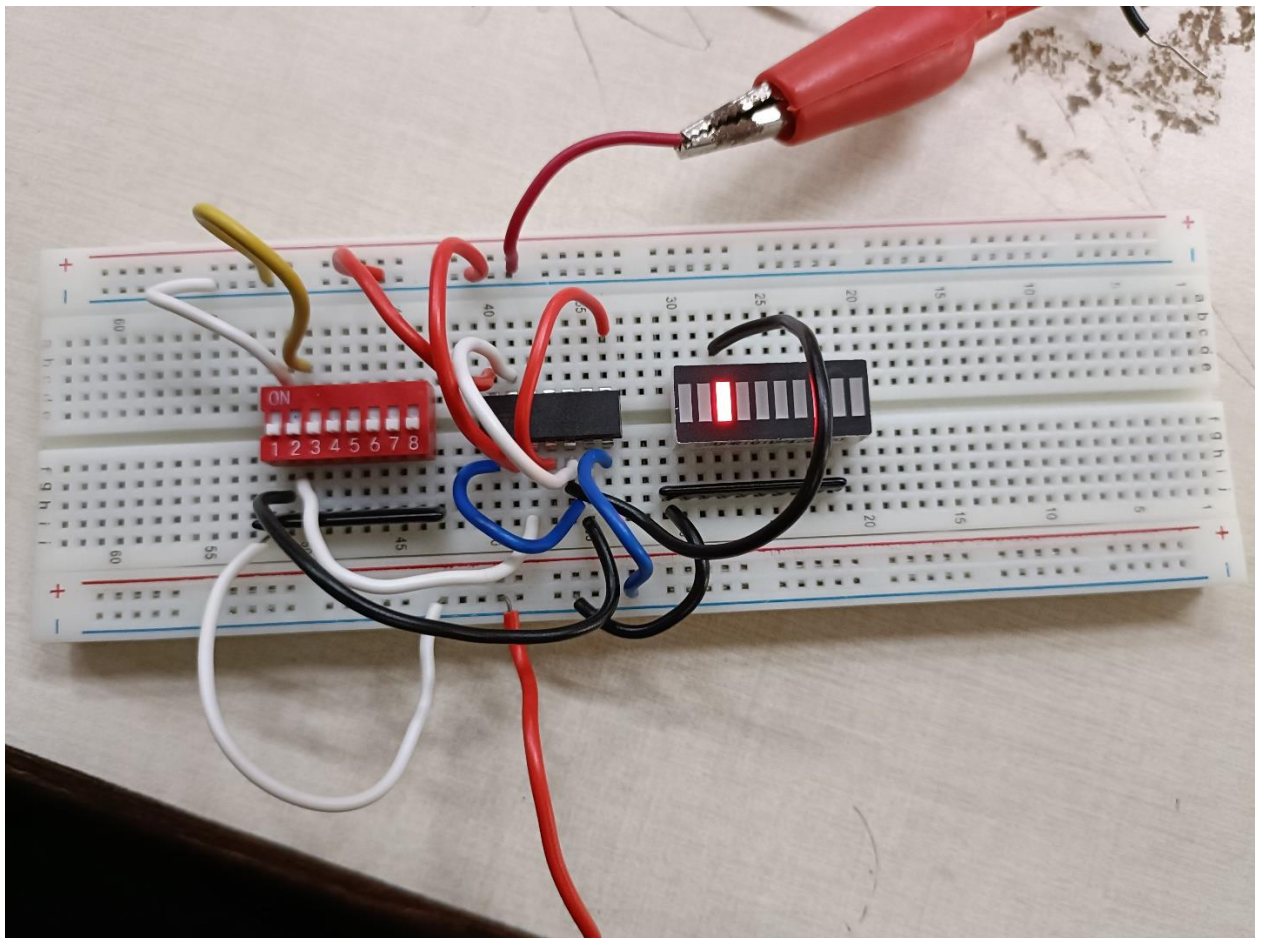



2)AND GATE (Snapshots & Circuit):

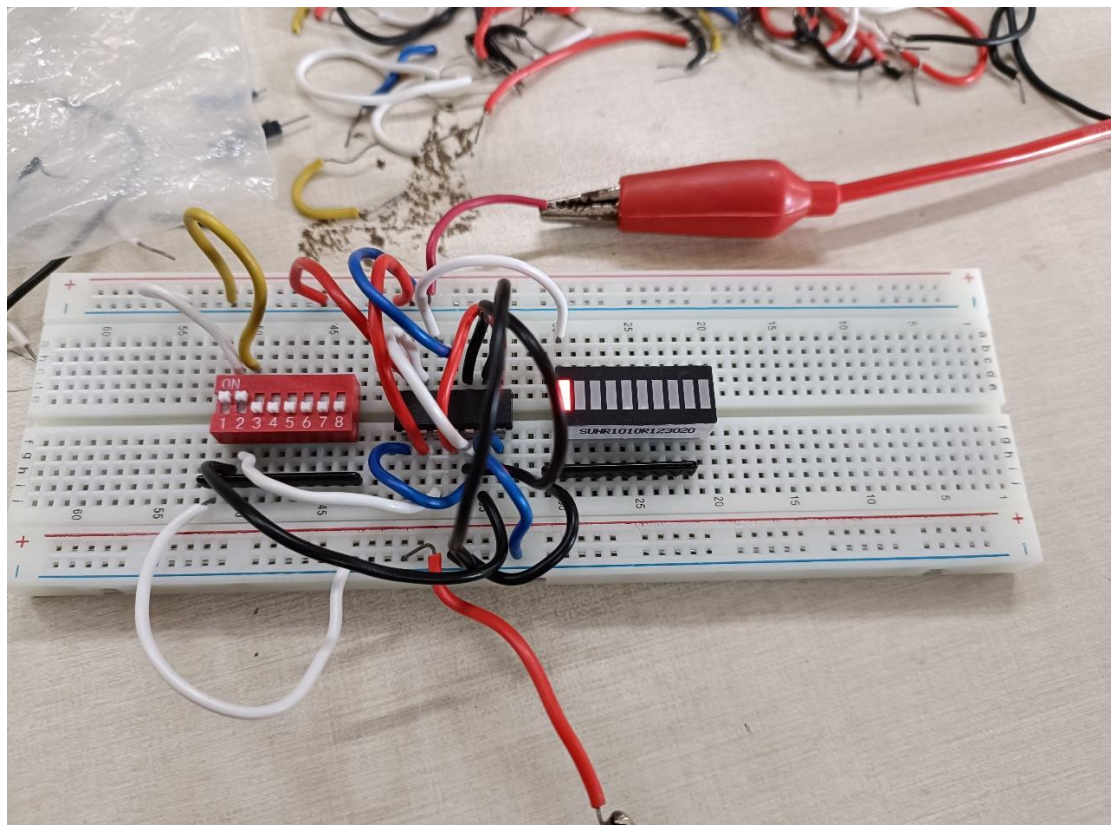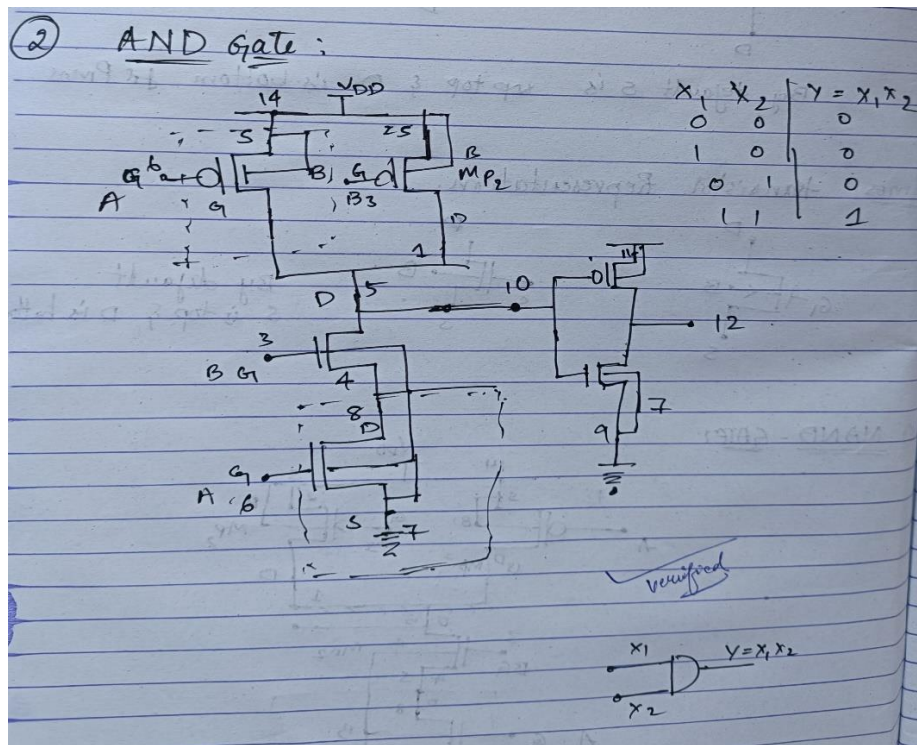

3) NOR GATE (Snapshot & Circuit):

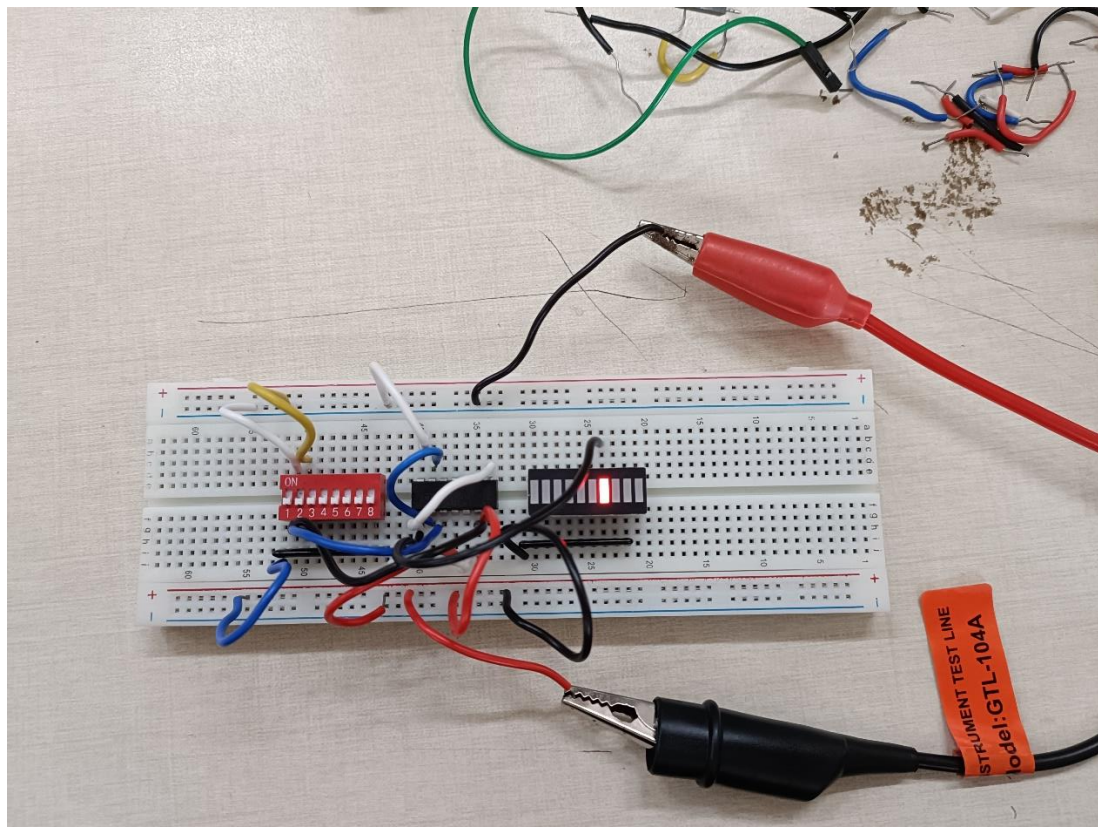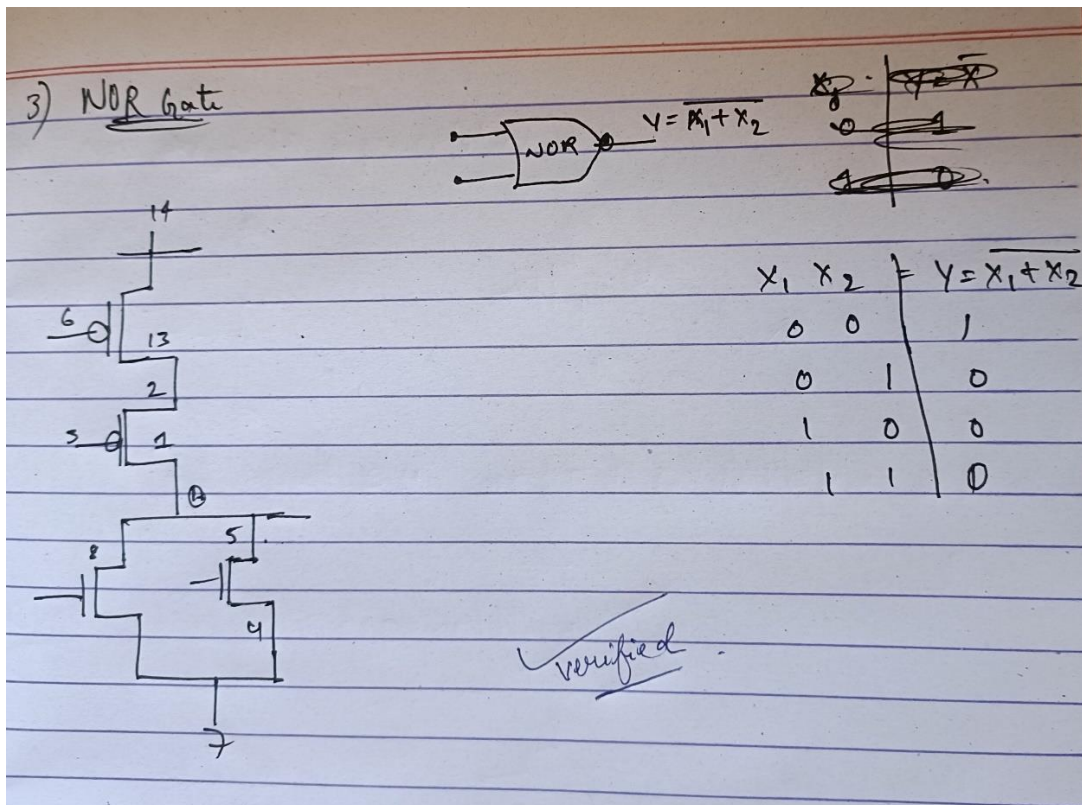

4) OR GATE (Snapshot & circuit) :

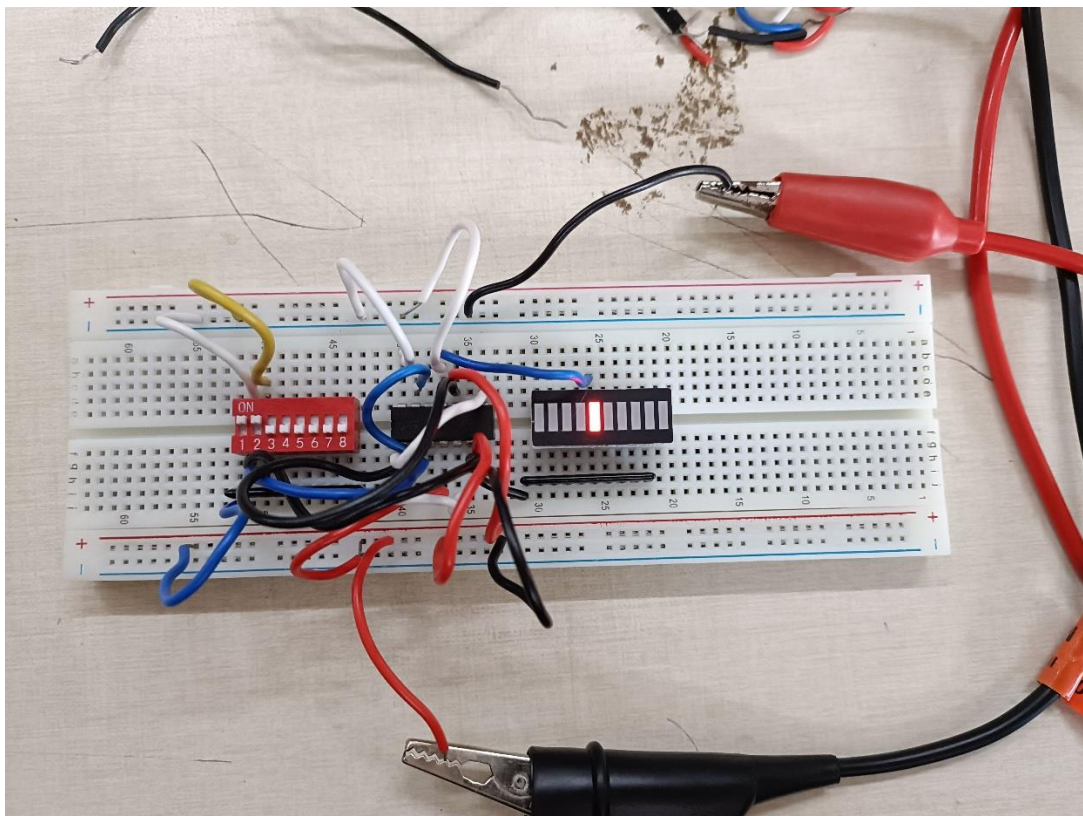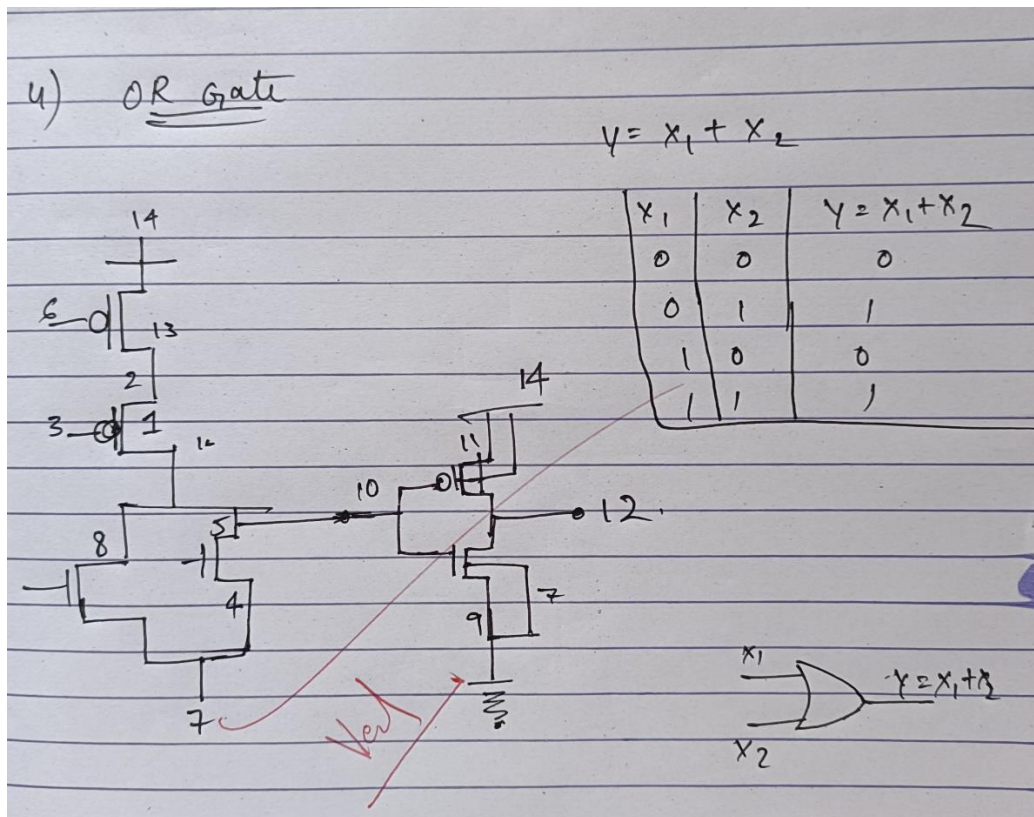

RESULTS :

Using this HCC4007UB IC which having 2 chanel of PMOS & NMOS we connected them in a circuit which results to form a CMOS and through that we form the different logic gates such as

NAND Gate

AND Gate

NOR Gate

OR Gate .

CONCLUSION :

Through this different IC's called HCC4007UB & HCF400UB which are acting as CMOS and forms some basic gates which finally gives a conclusion that we can connect any logic gate circuits using these PMOS & NMOS as ONE CMOS .