

# LAB 1 REPORT:

## STIMULATION OF IC's AS LOGIC GATES

**Aim:** Study of Digital ICs and basic components like power supply, DSO etc.

**Summary of the experiment:** Study of basic digital ICs and verifying their

functionality, learning the usage of function generator (FG) and digital storage

oscilloscope (DSO), and rigging up of circuits.

**Components used:** IC 7400,

IC 7408, IC 7432, IC 7486, 1Kohm resistor array -2 , DIP

switches, LED displays, breadboard, power supply.

### Design Procedure & circuit gates :

Truth table/Excitation table of all logic gates and logic circuits.


Truth tables are written below for :

- 1) NAND Gate
- 2) NOT Gate
- 3) AND Gate
- 4) XOR Gate
- 5) OR Gate .

## NAND Gate:

05/04/23  
NAND

① NOT + AND  
 $\overline{A \cdot B} = Y$

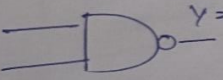A  B  $Y = \overline{A \cdot B}$

verified  
By Siddhant

NAND Gate (IC 7400)


A	B	$Y = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

## NOT Gate :

②

NOT gate . NO

$\overline{\overline{A}} \rightarrow \overline{A} = Y$

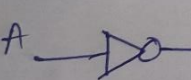A   $Y = \overline{A}$

NOR GATE (IC 7404)


A	$Y = \overline{A}$
0	1
1	0

verified

## AND Gate :

5/04/23

④ XOR GATE


A  B  $Y = A + B$

verified


XOR GATE (IC 7486)

A	B	$Y = A + B$
0	0	0
1	0	1
0	1	1
1	1	0

OR Gate :

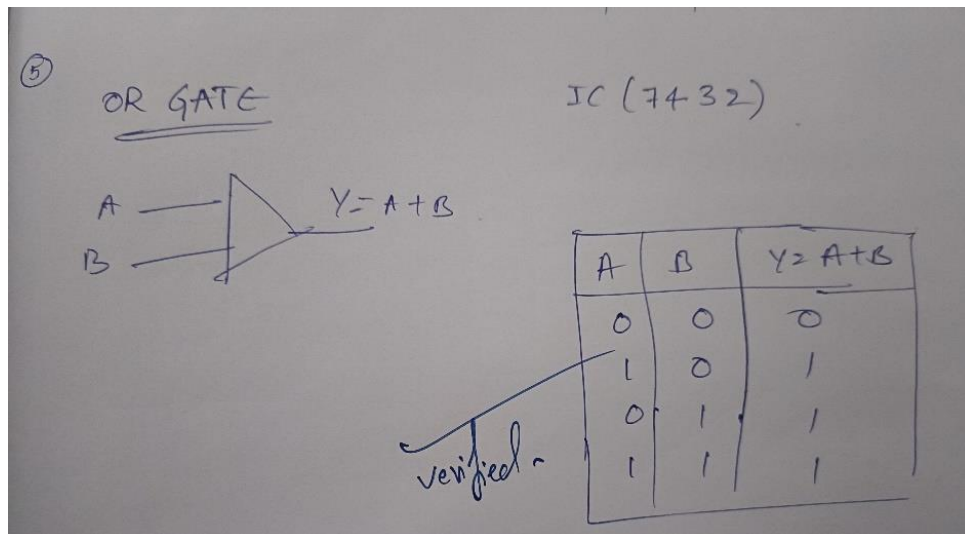


XOR Gate :

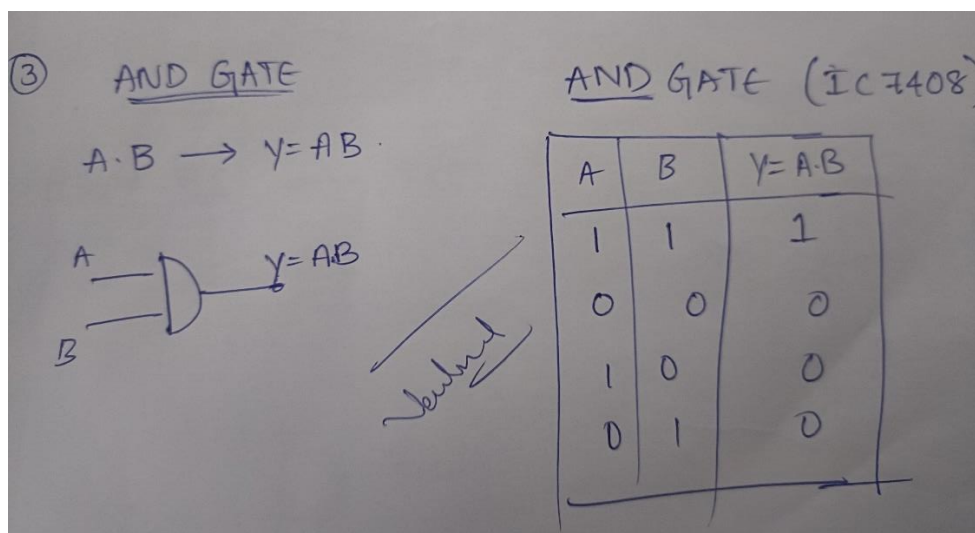


## Circuit and Simulation Snapshots:

1) IC 7404 – NOT GATE

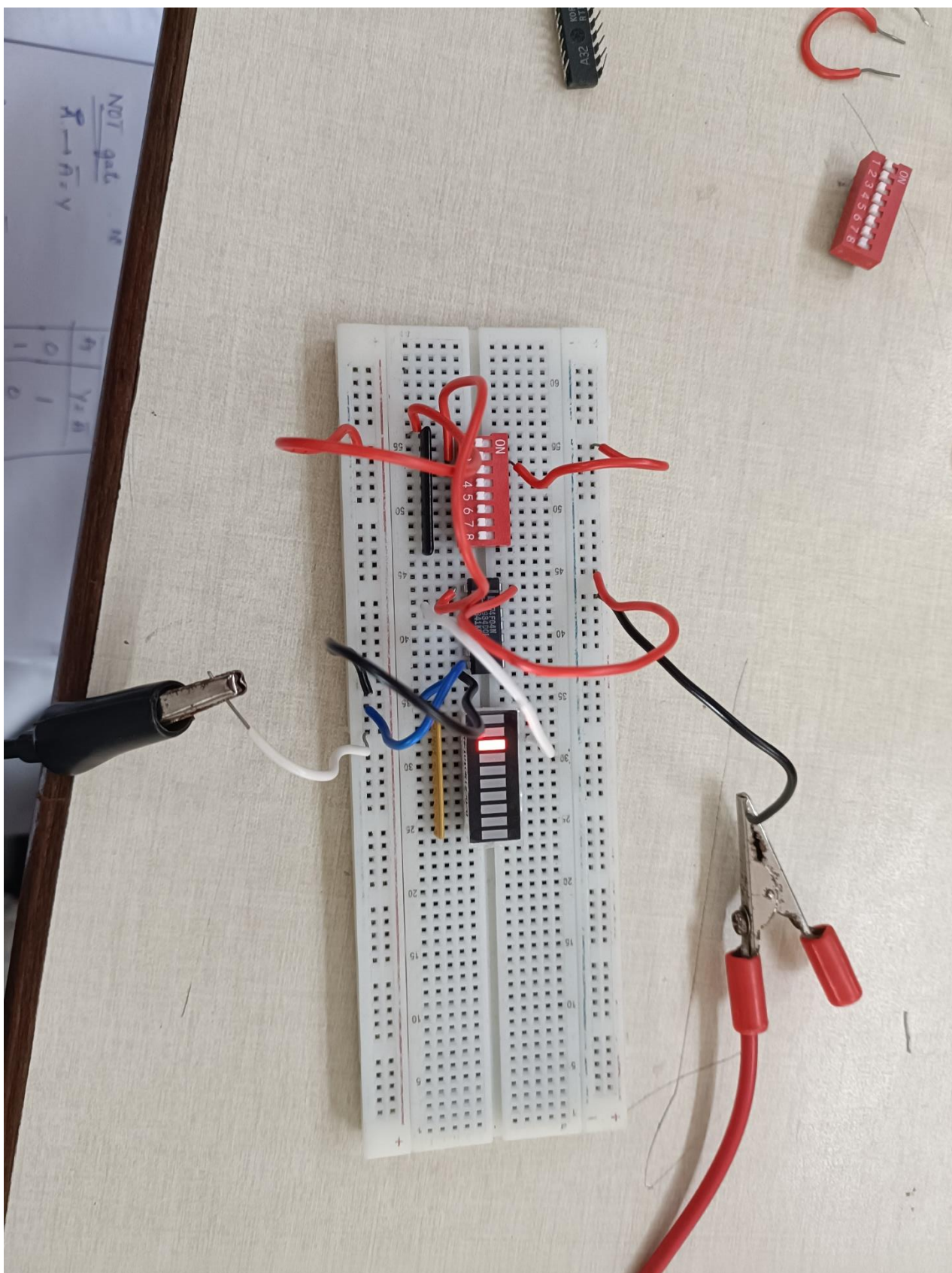




## 2) IC 7408 – XOR GATE

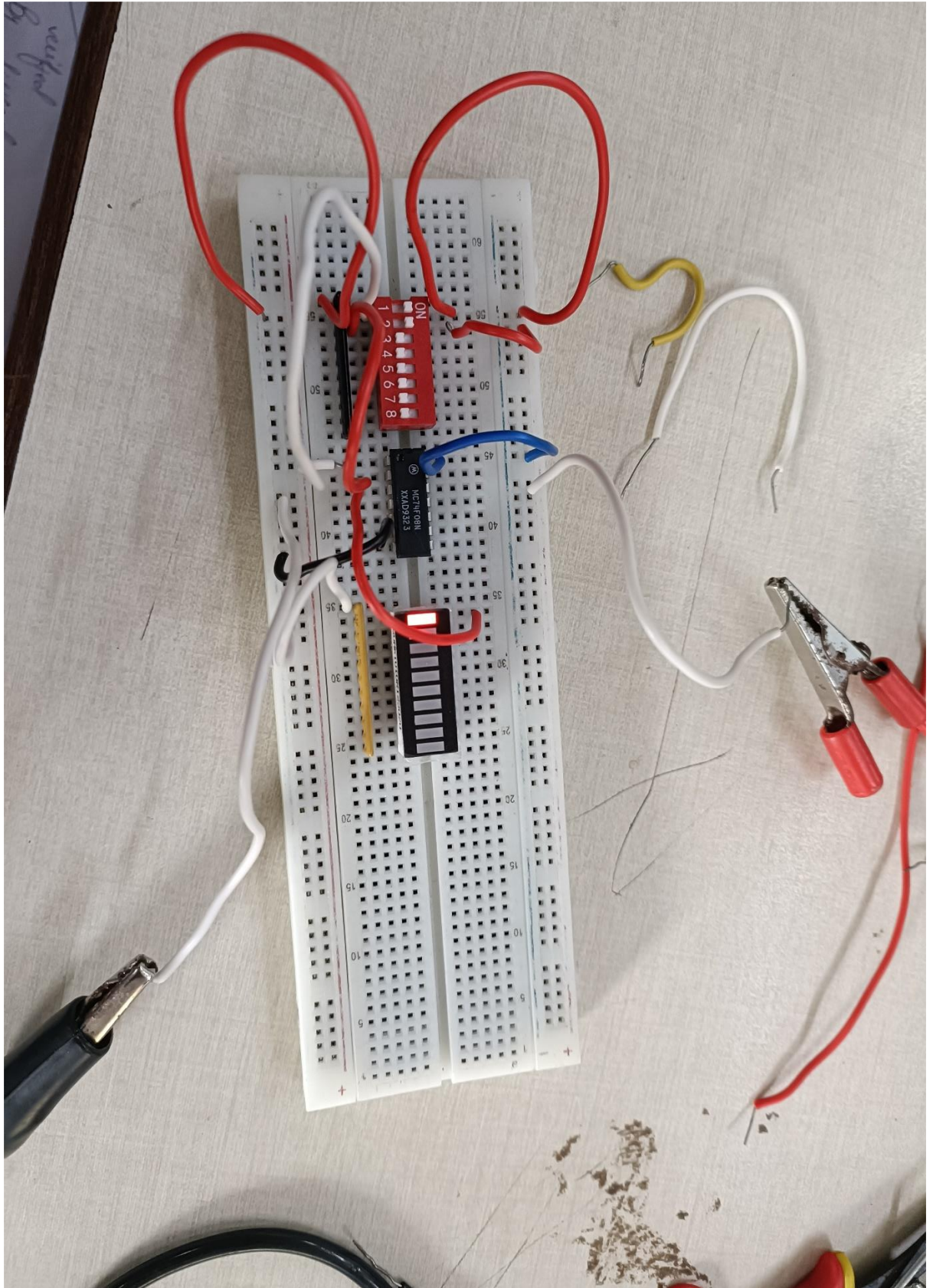


### 3) IC 7400 – NAND GATE

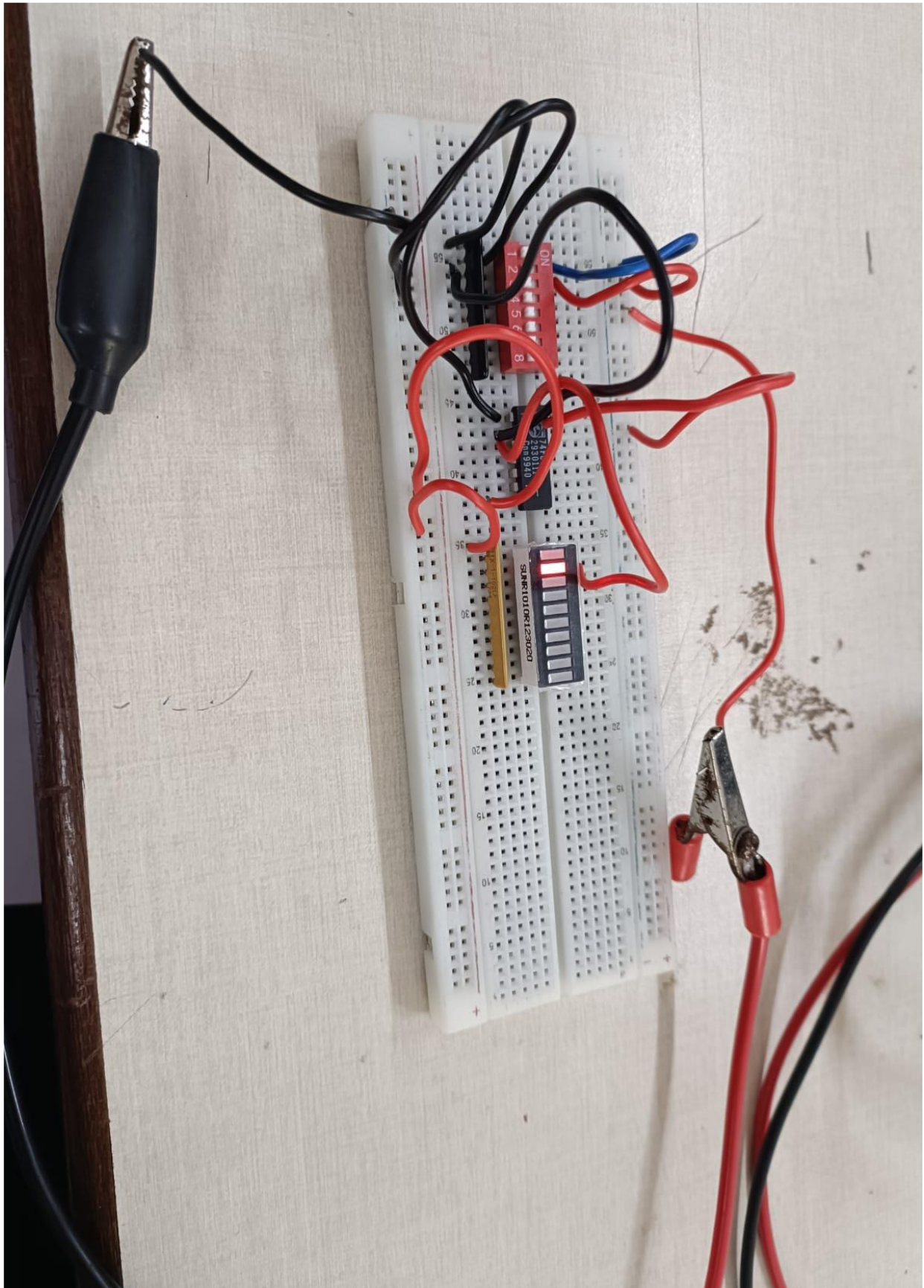




#### 4) IC 7432 – OR GATE

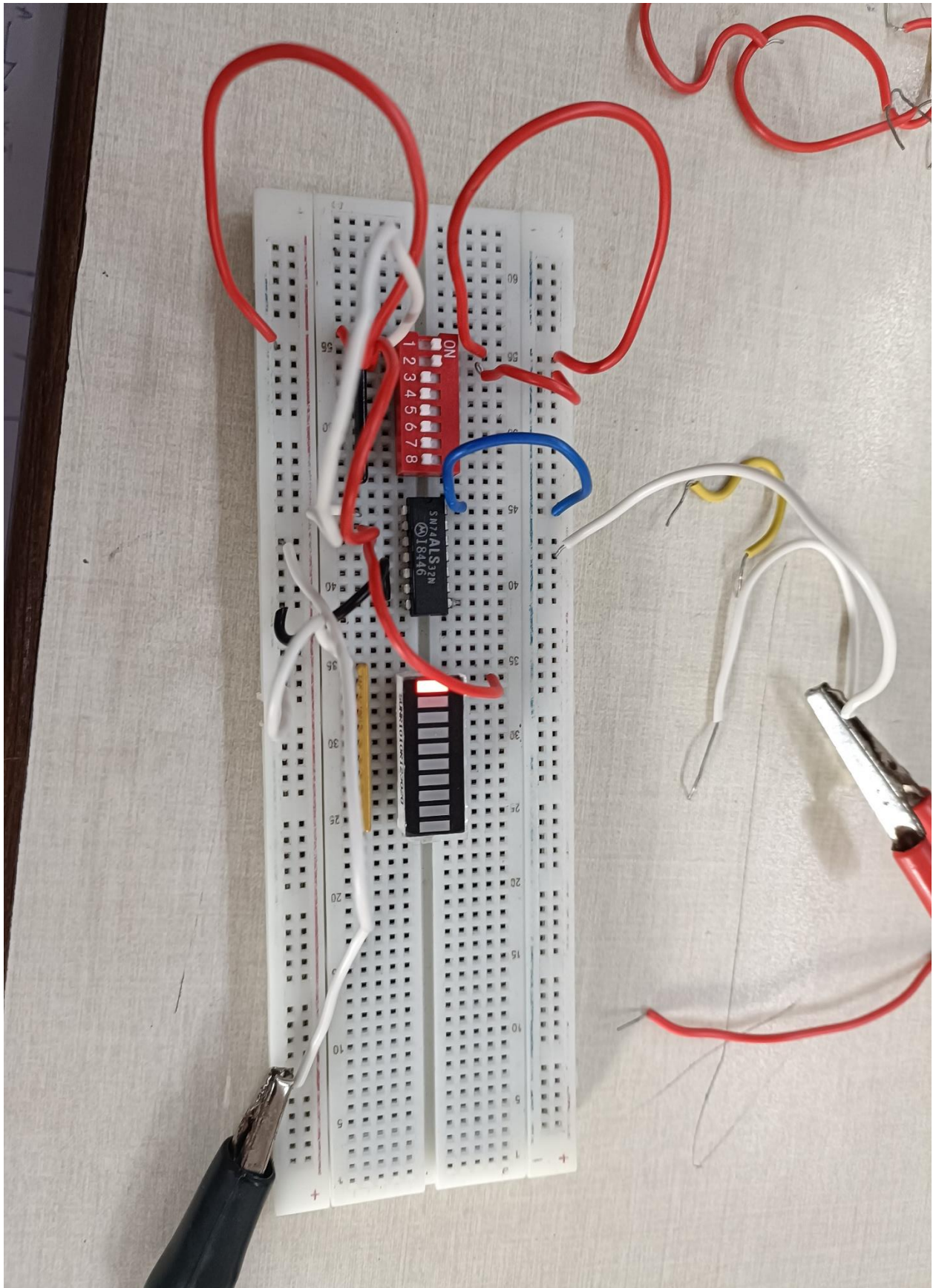

## 5) IC 7486 – AND GATE

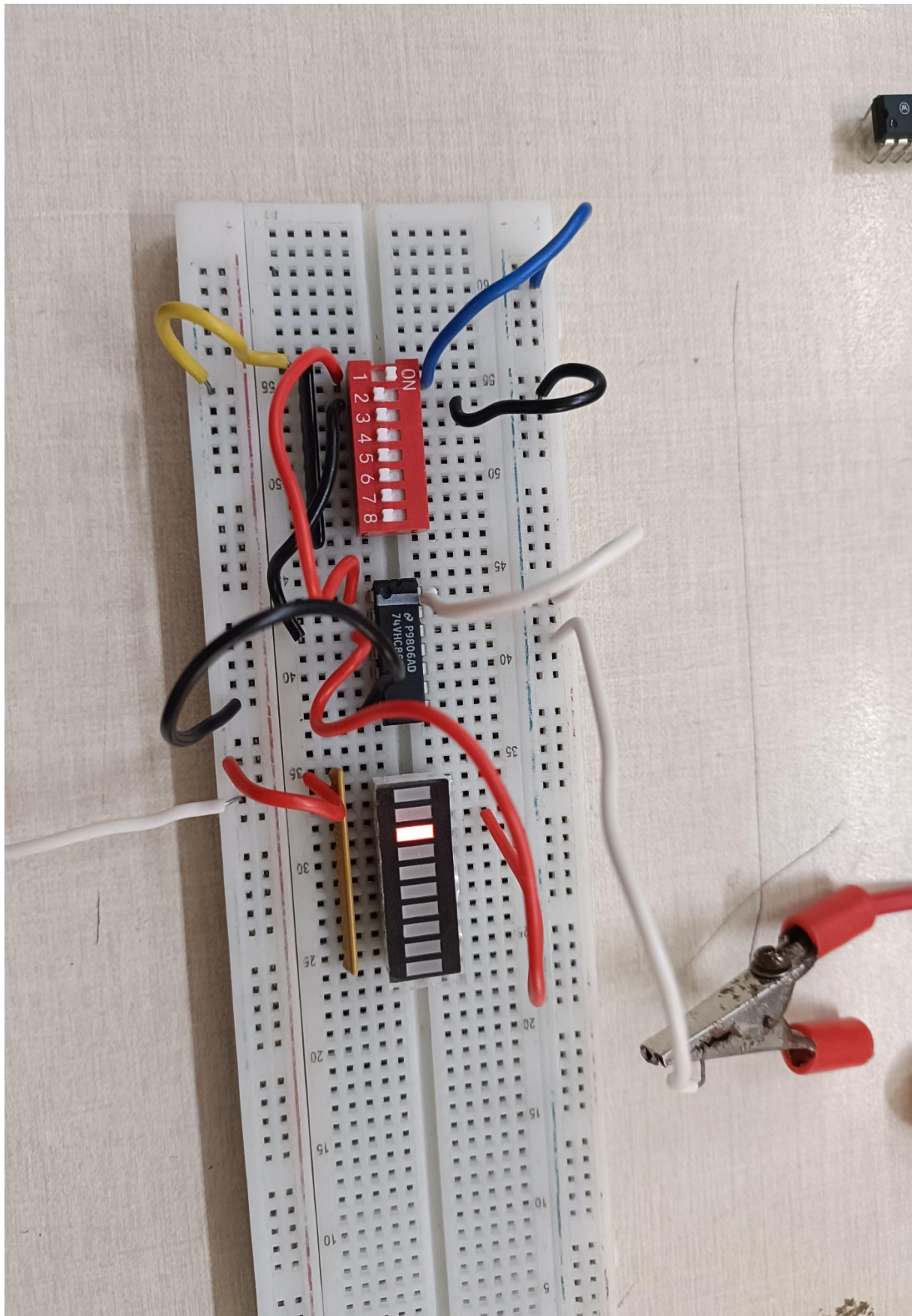



## RESULTS :

Using these IC's we connected them in a circuit which results to form the different logic gates such as

IC 7400 acts as NAND Gate

IC 7404 acts as NOT Gate

IC 7408 acts as AND Gate

IC 7486 acts as XOR Gate

IC 7432 acts as OR Gate .


## CONCLUSION :

Through these different IC's which are acting as different logic gates which finally gives a conclusion that we can connect any logic gate circuits using these IC's .

The below circuit diagram and logic gate with its truth table are attached, resulting in using two different IC's acts as two different gates .

Given gates as  $AB + BC$
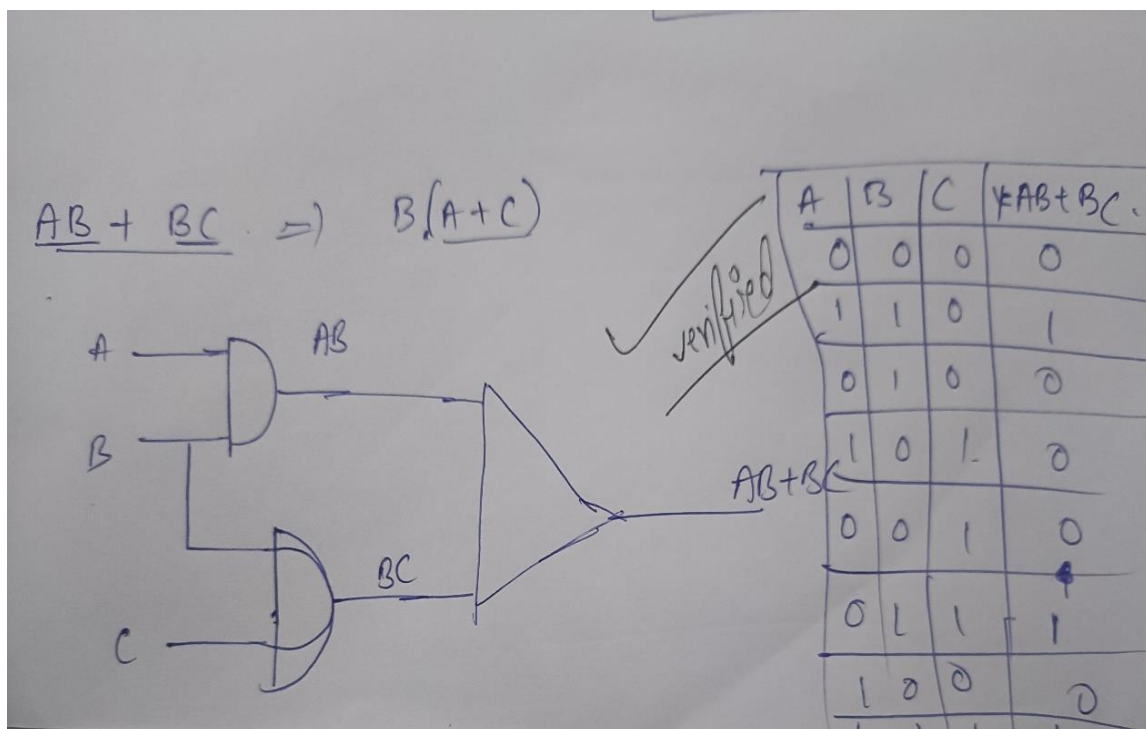
$$= B(A+C) \quad \{ \text{We are using two AND gates and a OR gate} \}$$



**Snapshot of this combination of gates with IC's :**

**IC 7408 & IC 7432**

