

# LAB 6 - REPORT

## For Q1)

### Aim:

An automobile alarm circuit is used to detect certain undesirable conditions. The three switches are used to indicate the status of door(D), the ignition(IS), and the headlights (HS), respectively.

Design a logic circuit with these switches as inputs so that the alarm(A) will be activated only whenever either of the following conditions exists:

- The headlights are ON while the ignition is OFF
- The door is open while the ignition is ON

### ➤ Implement The Above Circuit Using:

(1) A 3:8 decoder(74HC237IC) and suitable 2-input logic gates.

### Summary of the Experiment:

By writing the truth table, we form a logic equation with the output values for the given cases and then implement the circuit using a 3:8 decoder and OR gates.

### Components used:

Decoder 74HC237, IC 74ALS32 and 1Kohm resistor array, DIP switches, LED displays, breadboard, power supply.

### Design & Circuit diagram:

14/02/23

## Lab-6

Decoder

- ① 3 switches to indicate status of  
 door (D)  
 The ignition (IS)  
 the Headlight (HS)

The Alarm(A) will be activated when

- HS - on, IS - off
- D - open IS - on

D - open - logic 1  
 close - 0


IS - on - 1  
 off - 0

HS - on - 1  
 off - 0


E	inputs			(A) outputs										F
	D	IS	HS	F	y <sub>0</sub>	y <sub>1</sub>	y <sub>2</sub>	y <sub>3</sub>	y <sub>4</sub>	y <sub>5</sub>	y <sub>6</sub>	y <sub>7</sub>	=	
0	0	0	0	0	1	0	0	0	0	0	0	0	0	
	0	0	1	1	0	1	0	0	0	0	0	0	0	
	0	1	0	0	0	0	1	0	0	0	0	0	0	
	0	1	1	0	0	0	0	1	0	0	0	0	0	
	1	0	0	0	0	0	0	0	1	0	0	0	0	
	1	0	1	1	0	0	0	0	0	1	0	0	0	
	1	1	0	1	0	0	0	0	0	0	0	1	0	
	1	1	1	1	0	0	0	0	0	0	0	0	1	

Output A =  $\sum 1, 5, 6, 7$

$\sum y_1, y_5, y_6, y_7$

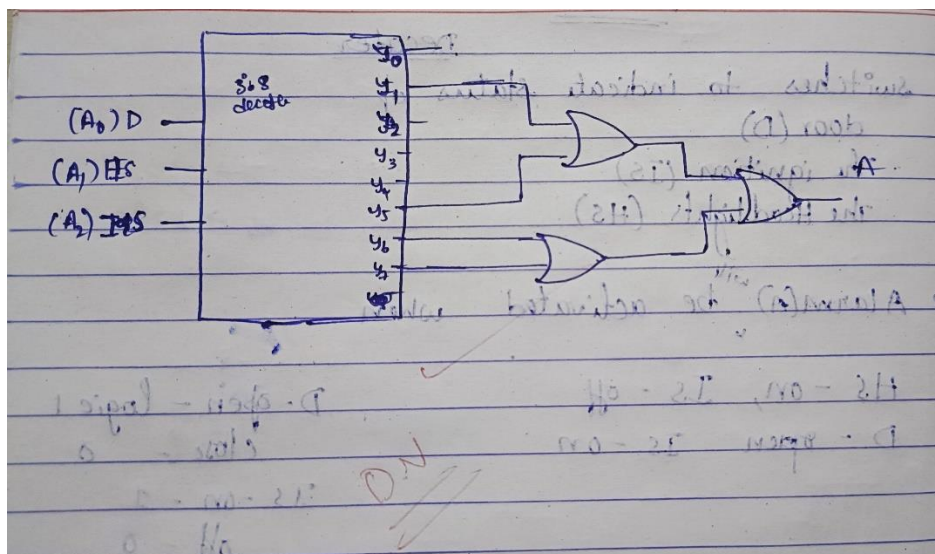

## Snapshots :

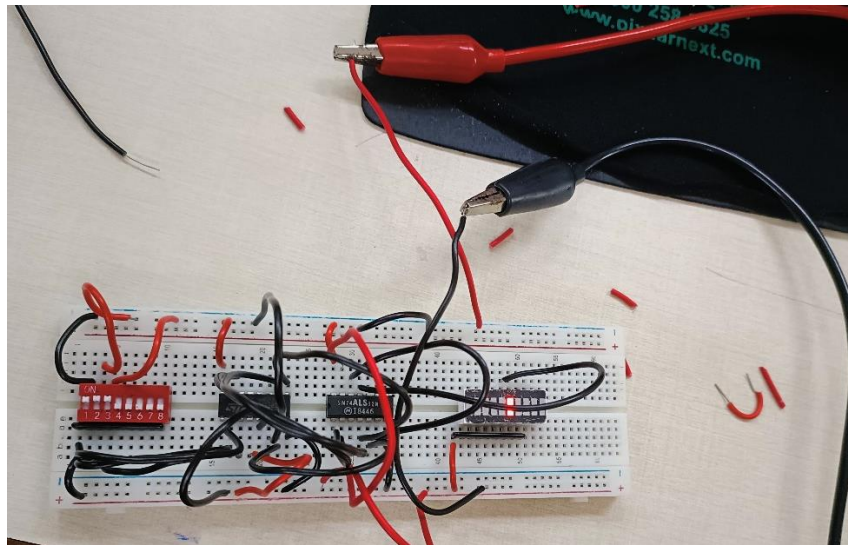

## Results and Conclusion:

I understood the properties of a decoder. I have learned how to form a logic equation using a truth table, and implement and build a circuit using DECODER. I have got the results perfectly with verified outputs.

\*\*\*\*

\*\*\*\*

For Q2)

## Aim :

1. Design and implement 4:1 MUX using basic logic gates.
2. Implement the following SOP with 4:1 MUX.

$$Y = f(A, B, C, D) = \sum m(3, 5, 7, 10, 12, 15) + d(9, 11, 13, 14)$$


## Summary of the experiment:

We implement a 4:1 multiplexer using basic logic gates and with the properties of DM74153 IC, we make the desired output.

## Components used:

DM74153 IC, IC 7408 and 1Kohm resistor array, DIP switches, LED displays, breadboard, power supply.

## Design & Circuit diagram:

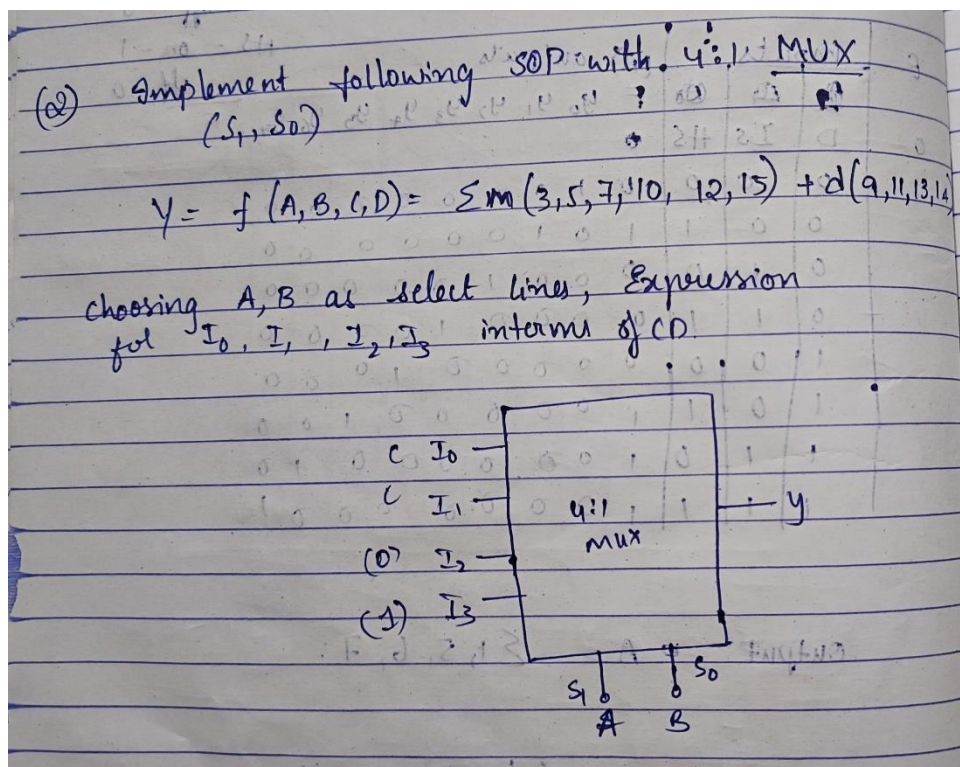



16/2/23


	[00] $\bar{A}\bar{B}$	[01] $\bar{A}B$	[10] $A\bar{B}$	[11] $AB$	...
$\bar{C}\bar{D}$ [00]	0	4	8	(12)	
$\bar{C}D$ [01]	1	(5)	X	X	
$C\bar{D}$ [10]	2	6	(10)	X	
$CD$ [11]	(3)	(7)	X	(15)	
	$I_0$	$I_1$	$I_2$	$I_3$	

$I_0 = \bar{C}\bar{D}$   
 $I_1 = \bar{C}D + C\bar{D} = \bar{C}(D + \bar{D}) = \bar{C}$   
 $I_2 = C\bar{D} + CD = C(\bar{D} + D) = C$   
 $I_3 = \bar{C}\bar{D} + C\bar{D} + C\bar{D} + \bar{C}D = 1$

A	B	Y
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

✓ DV

Snapshots :

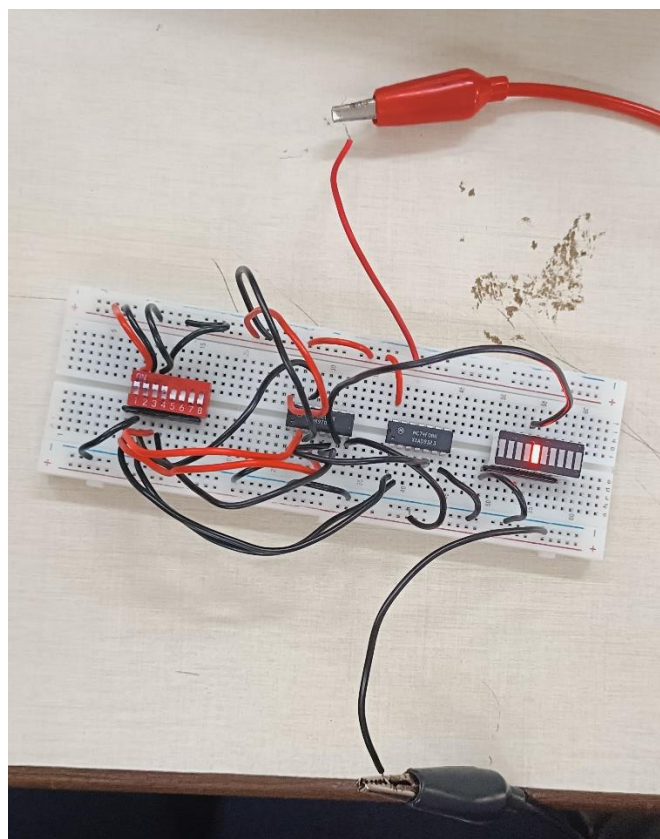

## Results & Conclusion :

- I understood the properties of DM74153 IC.
- Could implement and build a 4:1 MUX using basic logic gates by forming an equation using the truth table and got verified results for that.
- In the second part of the question, I was able build a the required output  $f(A, B, C, D) = \Sigma m(3,5,7,10,12,15) + d(9,11,13,14)$  using 4:1 MUX using DM74153 IC.
- I have learned the implementation working about multiplexer

**\*\*\* THE END\*\*\***